

# Week 2: Power and Equivalent Circuits

From last time:

- Ohm's Law:

$$\downarrow I \quad \begin{array}{c} + \\ \Delta V = IR \\ - \end{array}$$


- KVL:

$$\sum_{\text{LOOP}} V = 0$$

- KCL:

$$\sum_{\text{IN}} I = \sum_{\text{OUT}} I$$

- Series and Parallel Resistances:


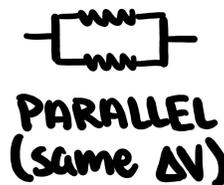


New for this week:

- Power (Watt's Law):


$$P_{\text{ABSORBED}} = \Delta V_{+ \rightarrow -} \cdot I$$

- Thevenin and Norton Equivalent:

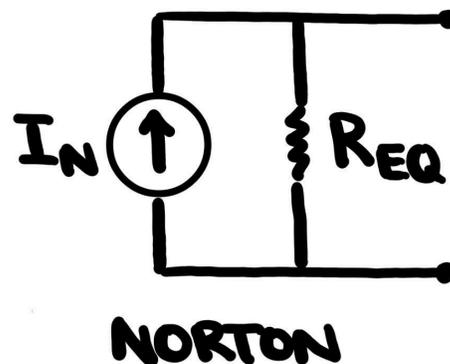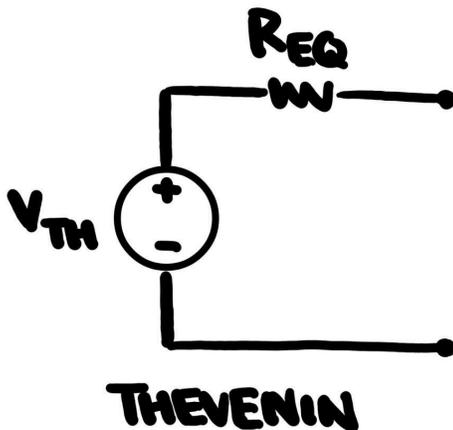

## Problems:

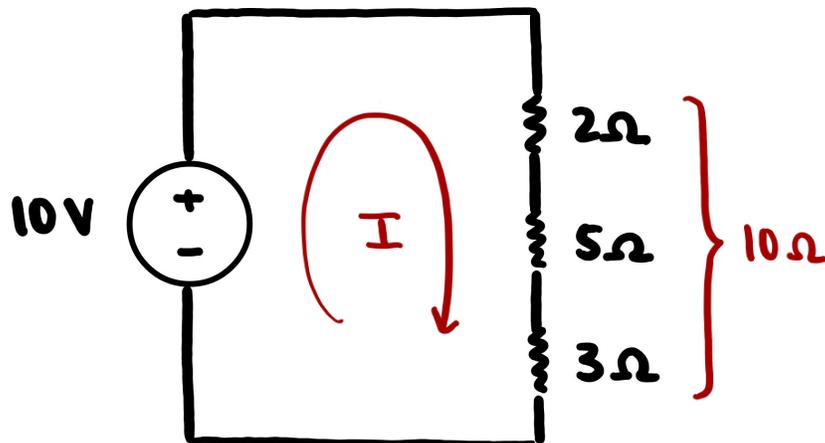1. **Power Predicament:** Use KVL, Ohm's Law, and Watt's Law to find the power generated/consumed by each source and resistor in the below circuit:



$$R_{\text{total}} = 2\Omega + 5\Omega + 3\Omega = 10\Omega$$

$$\Delta V_{\text{total}} = IR_{\text{total}} \rightarrow I = \frac{\Delta V_{\text{total}}}{R_{\text{total}}} = \frac{10\text{V}}{10\Omega} = 1\text{A}$$

by voltage division,  $\Delta V_{R_i} = \Delta V_{\text{total}} \left( \frac{R_i}{R_{\text{total}}} \right)$

$$\hookrightarrow \Delta V_{2\Omega} = 10\text{V} \left( \frac{2\Omega}{10\Omega} \right) = 2\text{V}$$


$$\hookrightarrow \Delta V_{5\Omega} = 10\text{V} \left( \frac{5\Omega}{10\Omega} \right) = 5\text{V}$$

$$\hookrightarrow \Delta V_{3\Omega} = 10\text{V} \left( \frac{3\Omega}{10\Omega} \right) = 3\text{V}$$

and so the dissipated/absorbed power for each resistor:


$$\begin{aligned} \hookrightarrow P_{2\Omega} &= 2\text{V} \cdot 1\text{A} = 2\text{W} \\ \hookrightarrow P_{5\Omega} &= 5\text{V} \cdot 1\text{A} = 5\text{W} \\ \hookrightarrow P_{3\Omega} &= 3\text{V} \cdot 1\text{A} = 3\text{W} \end{aligned}$$

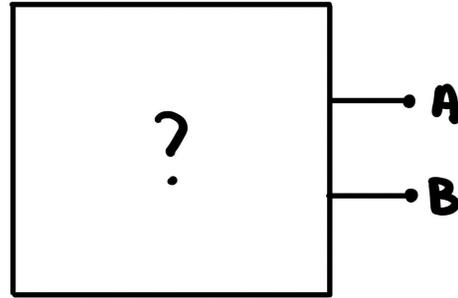2. **Black Box Bonanza:** Consider the black box at right, which contains a circuit with two terminals, A and B, to connect to the outside world. We find the open circuit voltage and short circuit current between the terminals to be 7.5 V and 2.5 A, respectively.




- Draw the Thevenin and Norton equivalent models of the internals of the black box. Compute the Thevenin voltage, Norton current, and equivalent resistance.
- Demonstrate that the two circuit models are equivalent by calculating the power dissipated by a  $2\ \Omega$  resistor connected between A and B.


**A) FOR THEVENIN:**

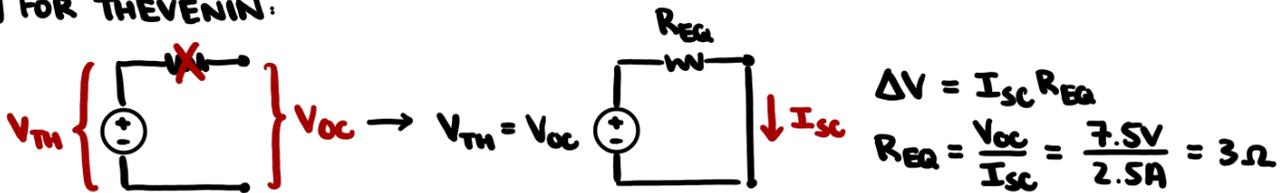


**FOR NORTON:**

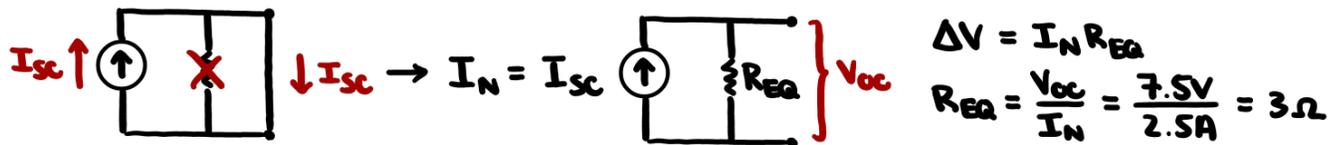

**THUS:**

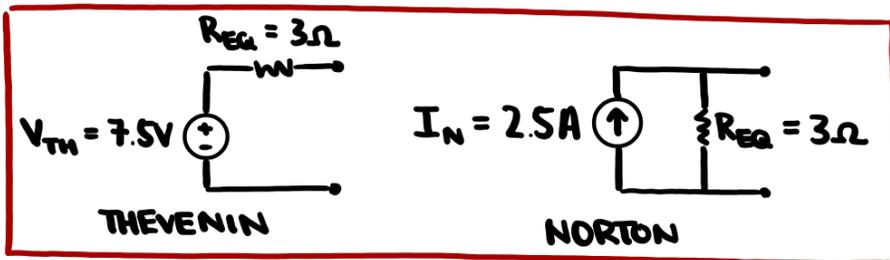

B) same P?

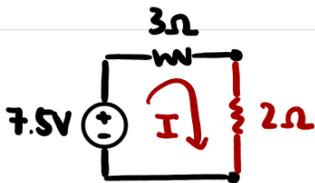

$$\Delta V = IR$$

$$I = \frac{\Delta V}{R} = \frac{7.5V}{5\Omega} = 1.5A$$

$$\Delta V_{2\Omega} = I \cdot 2\Omega$$

$$\Delta V_{2\Omega} = 1.5A \cdot 2\Omega$$

$$\Delta V_{2\Omega} = 3V$$

$$P_{\text{THEVENIN}} = \Delta V_{2\Omega} \cdot I = 3V \cdot 1.5A = 4.5W$$



$$3\Omega \parallel 2\Omega = \frac{1}{\frac{1}{3\Omega} + \frac{1}{2\Omega}} = 1.2\Omega$$


$$\Delta V = IR = 2.5A \cdot 1.2\Omega = 3V$$

$$\hookrightarrow I = \frac{\Delta V_{2\Omega}}{2\Omega} = \frac{3V}{2\Omega} = 1.5A$$


$$P_{\text{NORTON}} = \Delta V_{2\Omega} \cdot I = 3V \cdot 1.5A = 4.5W$$

SAME, YAY! :D

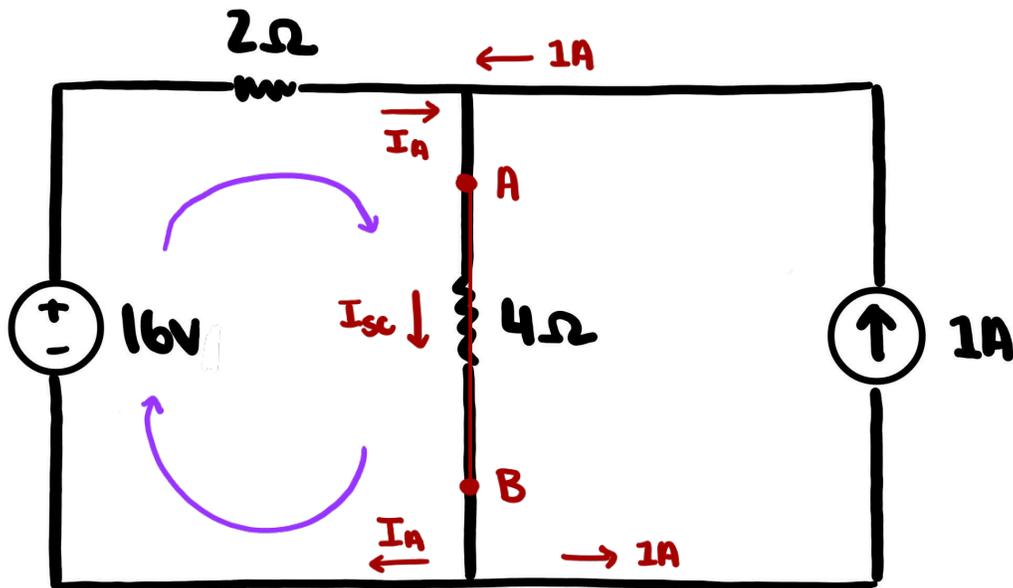3. **Recitation Roadblock, Revisited:** Remember this tricky problem from last week? Use either a Thevenin or Norton equivalent circuit to simplify this circuit and solve for the voltage across and current through the center  $4\ \Omega$  resistor.



- What is  $V_{oc}$ ?

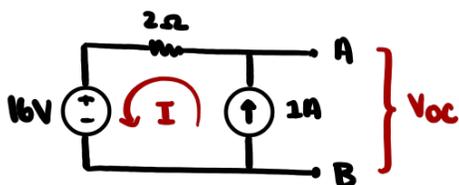

by KVL:  $-16V - I \cdot 2\Omega + V_{oc} = 0$

$$V_{oc} = 16V + 2V$$

$$V_{oc} = 18V$$

- what is  $I_{sc}$ ? see above KCL drawings...

$$I_{sc} = I_A + 1A$$

via purple KVL loop.  $16V - I_A \cdot 2\Omega = 0A$

$$I_A \cdot 2\Omega = 16V$$


$$I_A = \frac{16V}{2\Omega} = 8A$$

$$I_{sc} = 9A$$

- Thevenin Equivalent:

$$V_{TH} = V_{OC} = 18V$$
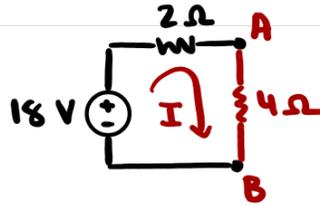
$$R_{EQ} = \frac{V_{OC}}{I_{SC}} = \frac{18V}{9A} = 2\Omega$$



- then use KVL to find desired voltage/current:

$$\Delta V = IR$$


$$I = \frac{\Delta V}{R} = \frac{18V}{6\Omega} = 3A$$

$$\Delta V = IR = 3A \cdot 4\Omega = 12V$$


$$\begin{array}{l} I_{4\Omega} = 3A \\ \Delta V_{4\Omega} = 12V \end{array}$$

4. **(Bonus!) A Couple Challenge Problems:** The following are a few complex (taken from David's 18-220!) questions to probe your understanding of resistor networks, voltage/current division, and Norton/Thevenin equivalent circuits!

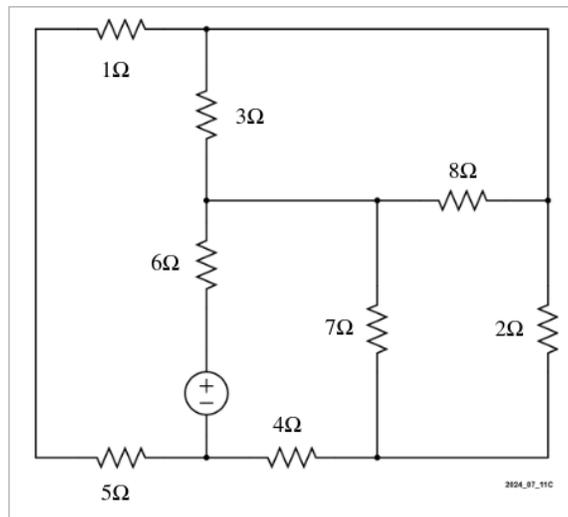- a. Simplify the following network of resistors as much as you can: what values of resistors can be safely considered in series? Parallel?





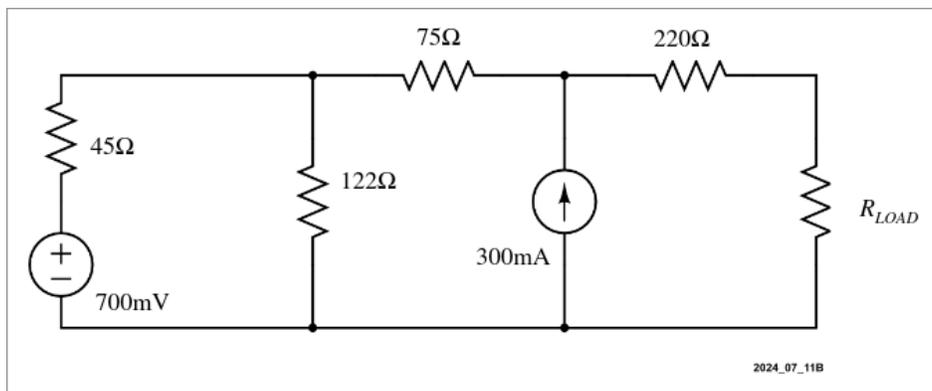- b. Find the Thevenin equivalent of the following circuit with respect to the load resistor (*hint: it may be useful to look up a technique called "superposition" - you won't need it in this class, but it's an interesting alternative method of solving more complex circuits!*):



- c. Call Kesden/David over and ask any questions you might have about ECE, life at CMU, job search, anything at all! :)

A)

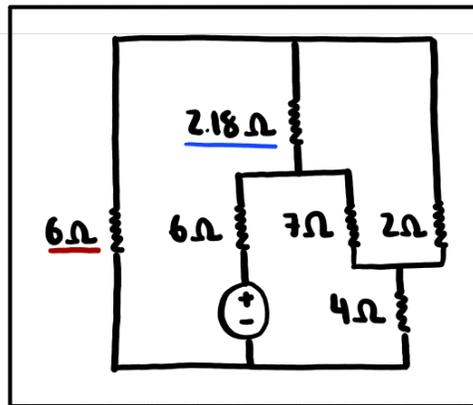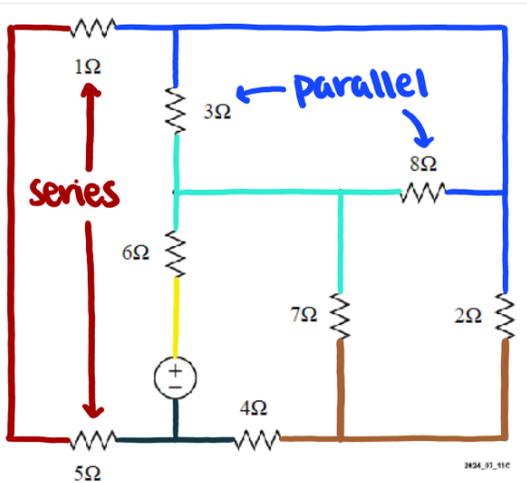


series:  $5\Omega + 1\Omega = 6\Omega$

parallel:  $3\Omega \parallel 8\Omega = \frac{1}{\frac{1}{3\Omega} + \frac{1}{8\Omega}} \approx 2.18\Omega$


B)

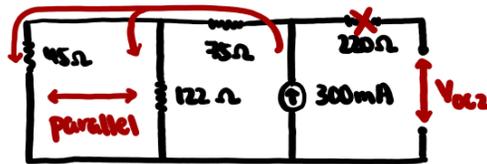want to find  $V_{oc}$ ,  $I_{sc}$  start with finding  $V_{oc}$  via superposition:



$$V_{oc1} = V_s \cdot \frac{R_2}{R_1 + R_2}$$
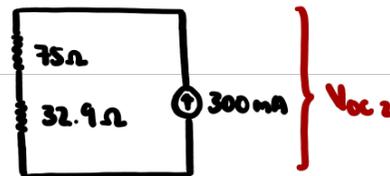
$$V_{oc1} = 700 \cdot 10^{-3} \cdot \frac{122}{167} = 511 \text{ mV}$$



$$\Delta V = IR$$

$$V_{oc2} = (300 \cdot 10^{-3})(107.9)$$




$$V_{oc2} = 32.4 \text{ V}$$

$$V_{oc} = V_{oc1} + V_{oc2}$$

$$V_{oc} = 511 \cdot 10^{-3} + 32.4$$

$$V_{oc} = 32.9 \text{ V}$$


now find  $I_{sc}$  by the same method:

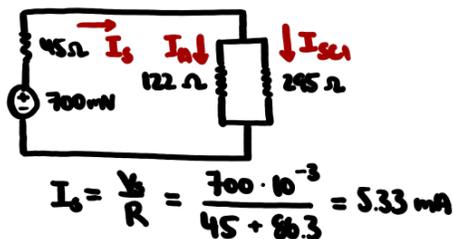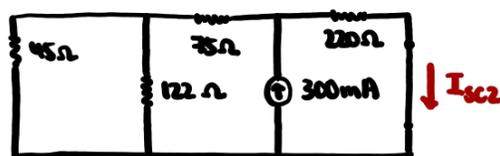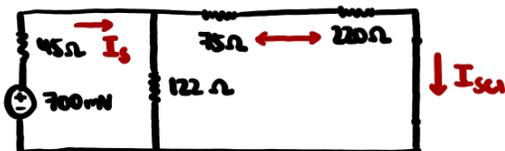

$$I_s = \frac{V_s}{R} = \frac{700 \cdot 10^{-3}}{45 + 86.3} = 5.33 \text{ mA}$$

$$I_s = I_{sc} + I_n$$
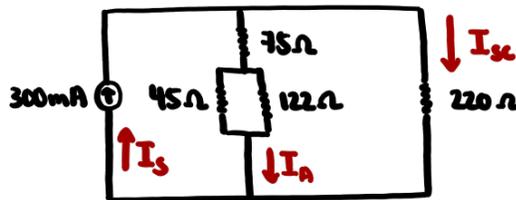
$$V_n = V_{sc1} = I_s \cdot R_{nec} = 5.33 \cdot 10^{-3} \cdot 86.3 = 460 \text{ mV}$$



$$V_n = V_{sc} ; I_s = I_n + I_{sc}$$

$$R_n = 75 + \frac{1}{\frac{1}{45} + \frac{1}{122}} = 108 \Omega$$

$$\Delta V = IR$$

$$I_{sc1} = \frac{\Delta V_{sc1}}{R}$$

$$I_{sc1} = \frac{460 \cdot 10^{-3}}{295} = 1.56 \text{ mA}$$

$$I_{sc} = I_{sc1} + I_{sc2}$$

$$I_{sc} = 1.56 \cdot 10^{-3} + 98.7 \cdot 10^{-3} = 100 \text{ mA}$$

$$I_s = I_n + I_{sc}$$

$$I_n(108) = I_{sc}(220)$$

$$I_n = I_s - I_{sc}$$

$$(I_s - I_{sc2}) \cdot 108 = I_{sc}(220)$$

$$I_{sc2} = \frac{108}{328} \cdot (300 \cdot 10^{-3}) = 98.7 \text{ mA}$$

finally. use ohm's law to get the thevenin equivalent

$$\Delta V = IR \rightarrow R = \frac{\Delta V}{I} = \frac{32.8}{100 \cdot 10^{-3}} = 328 \Omega$$

