

# Week 2: Power and Equivalent Circuits

From last time:

- Ohm's Law:

$$\downarrow I \quad \begin{array}{c} + \\ \Delta V = IR \\ - \end{array}$$


- KVL:

$$\sum_{\text{LOOP}} V = 0$$

- KCL:

$$\sum_{\text{IN}} I = \sum_{\text{OUT}} I$$

- Series and Parallel Resistances:


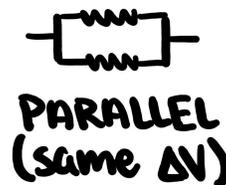


New for this week:

- Power (Watt's Law):


$$P_{\text{ABSORBED}} = \Delta V_{+ \rightarrow -} \cdot I$$

- Thevenin and Norton Equivalent:

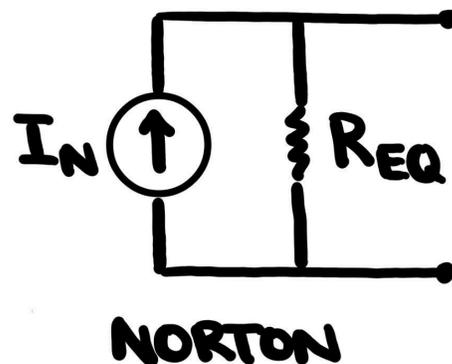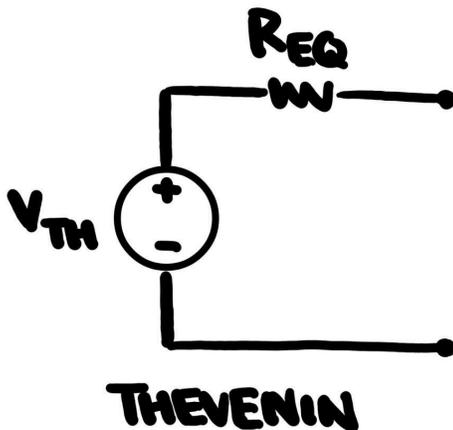


## Problems:

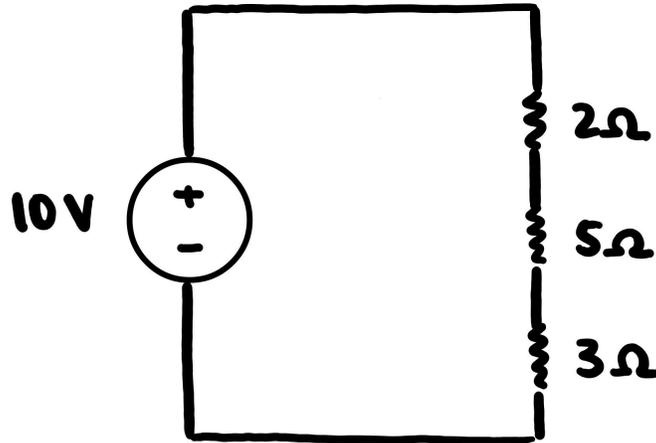1. **Power Predicament:** Use KVL, Ohm's Law, and Watt's Law to find the power generated/consumed by each source and resistor in the below circuit:




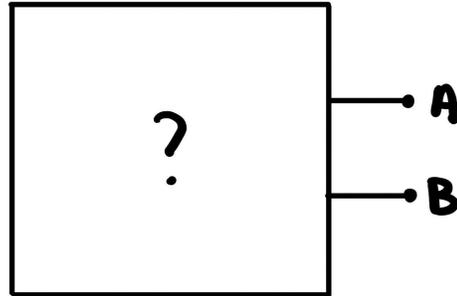2. **Black Box Bonanza:** Consider the black box at right, which contains a circuit with two terminals, A and B, to connect to the outside world. We find the open circuit voltage and short circuit current between the terminals to be 7.5 V and 2.5 A, respectively.




- Draw the Thevenin and Norton equivalent models of the internals of the black box. Compute the Thevenin voltage, Norton current, and equivalent resistance.
- Demonstrate that the two circuit models are equivalent by calculating the power dissipated by a  $2\ \Omega$  resistor connected between A and B.

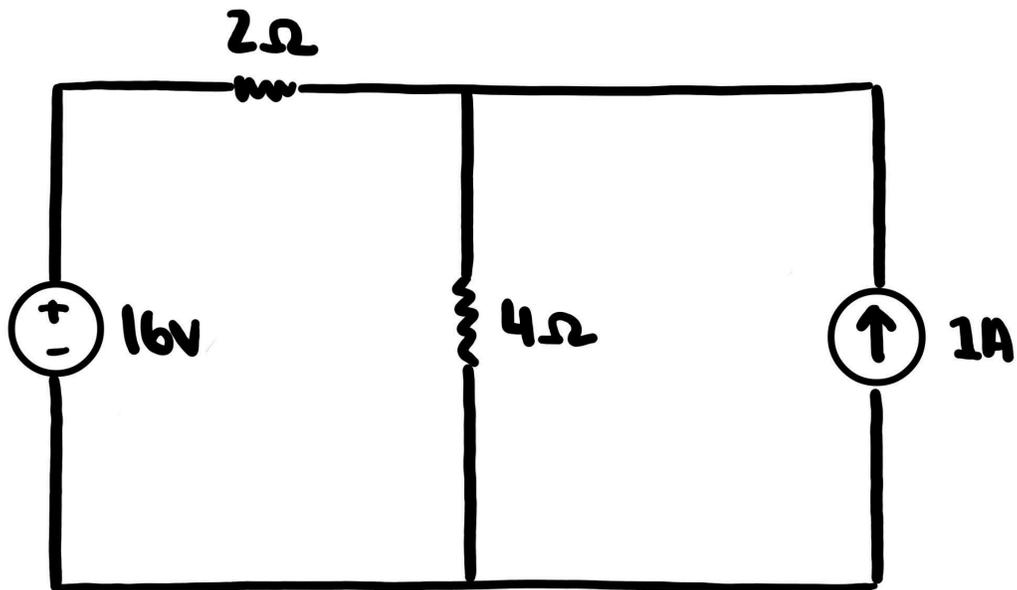3. **Recitation Roadblock, Revisited:** Remember this tricky problem from last week? Use either a Thevenin or Norton equivalent circuit to simplify this circuit and solve for the voltage across and current through the center  $4\ \Omega$  resistor.




4. **(Bonus!) A Couple Challenge Problems:** The following are a few complex (taken from David's 18-220!) questions to probe your understanding of resistor networks, voltage/current division, and Norton/Thevenin equivalent circuits!

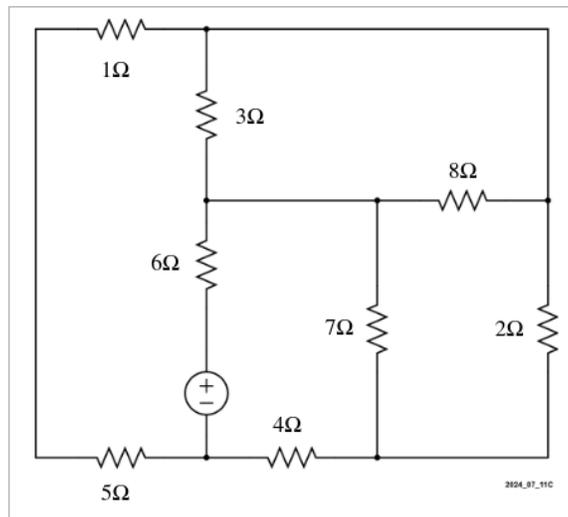- a. Simplify the following network of resistors as much as you can: what values of resistors can be safely considered in series? Parallel?



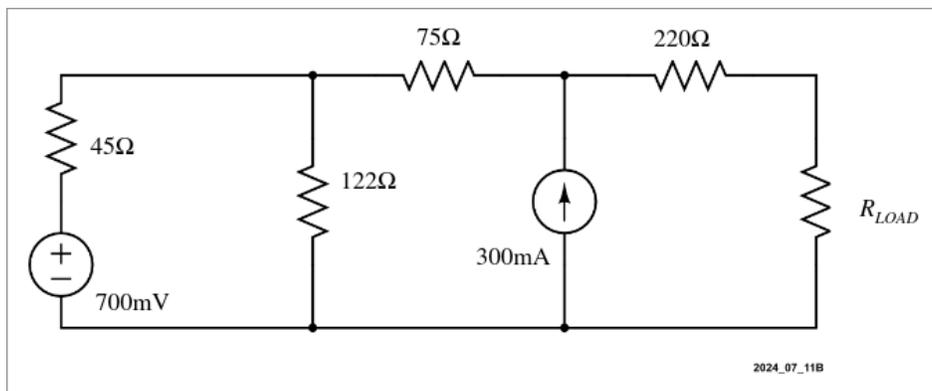- b. Find the Thevenin equivalent of the following circuit with respect to the load resistor (*hint: it may be useful to look up a technique called "superposition" - you won't need it in this class, but it's an interesting alternative method of solving more complex circuits!*):



- c. Call Kesden/David over and ask any questions you might have about ECE, life at CMU, job search, anything at all! :)